

CIRCUITS AND ELECTRONICS LABORATORY



Ramakrishnan Kalyanaraman
Cañada College

Circuits & Electronics Laboratory

Welcome to the Engineering Library. This Living Library is a principal hub of the [LibreTexts project](#), which is a multi-institutional collaborative venture to develop the next generation of open-access texts to improve postsecondary education at all levels of higher learning. The LibreTexts approach is highly collaborative where an Open Access textbook environment is under constant revision by students, faculty, and outside experts to supplant conventional paper-based books.

TABLE OF CONTENTS

Licensing

1: Lab Introduction

- 1.1: Lab Safety and Tools
- 1.2: Scientific and Engineering Notation
- 1.3: Laboratory Reports
- 1.4: DC Sources and Metering
 - 1.4.1: Theory Overview
 - 1.4.2: Equipment
 - 1.4.3: Procedure
 - 1.4.4: Data Tables
 - 1.4.5: Questions
- 1.5: Component Identification

2: Resistors

- 2.1: Theory Overview
- 2.2: Equipment
- 2.3: Procedure
- 2.4: Data Tables
- 2.5: Questions
- 2.6: Ohm's Law
 - 2.6.1: Theory Overview
 - 2.6.2: Equipment
 - 2.6.3: Schematic
 - 2.6.4: Procedure
 - 2.6.5: Data Tables
 - 2.6.6: Questions

3: Resistor Combinations

- 3.1: Series DC Circuits
 - 3.1.1: Theory Overview
 - 3.1.2: Equipment
 - 3.1.3: Schematics
 - 3.1.4: Procedure
 - 3.1.5: Data Tables
 - 3.1.6: Questions
- 3.2: Parallel DC Circuits
 - 3.2.1: Theory Overview
 - 3.2.2: Equipment
 - 3.2.3: Schematics
 - 3.2.4: Procedure
 - 3.2.5: Data Tables
 - 3.2.6: Questions
- 3.3: Series-Parallel DC Circuits
 - 3.3.1: Theory Overview

- 3.3.2: Equipment
- 3.3.3: Schematics
- 3.3.4: Procedure
- 3.3.5: Data Tables
- 3.3.6: Questions
- 3.4: Ladders and Bridges
 - 3.4.1: Theory Overview
 - 3.4.2: Equipment
 - 3.4.3: Schematics
 - 3.4.4: Procedure
 - 3.4.5: Data Tables
 - 3.4.6: Questions
- 3.5: Potentiometers and Rheostats
 - 3.5.1: Theory Overview
 - 3.5.2: Equipment
 - 3.5.3: Schematics
 - 3.5.4: Procedure
 - 3.5.5: Data Tables
 - 3.5.6: Questions

4: Theorems and Analysis Methods

- 4.1: Superposition Theorem
 - 4.1.1: Theory Overview
 - 4.1.2: Equipment
 - 4.1.3: Schematics
 - 4.1.4: Procedure
 - 4.1.5: Data Tables
 - 4.1.6: Questions
- 4.2: Thévenin's Theorem
 - 4.2.1: Theory Overview
 - 4.2.2: Equipment
 - 4.2.3: Schematics
 - 4.2.4: Procedure
 - 4.2.5: Data Tables
 - 4.2.6: Questions
- 4.3: Maximum Power Transfer
 - 4.3.1: Theory Overview
 - 4.3.2: Equipment
 - 4.3.3: Schematics
 - 4.3.4: Procedure
 - 4.3.5: Data Tables
 - 4.3.6: Questions
- 4.4: Nodal Analysis
 - 4.4.1: Theory Overview
 - 4.4.2: Equipment
 - 4.4.3: Schematics
 - 4.4.4: Procedure
 - 4.4.5: Data Tables
 - 4.4.6: Questions
- 4.5: Mesh Analysis

- 4.5.1: Theory Overview
- 4.5.2: Equipment
- 4.5.3: Schematics
- 4.5.4: Procedure
- 4.5.5: Data Tables
- 4.5.6: Questions

5: Time-dependent and AC Signals and Circuits

- 5.1: The Oscilloscope
 - 5.1.1: Theory Overview
 - 5.1.2: Equipment
 - 5.1.3: Components
 - 5.1.4: Schematics and Diagrams
 - 5.1.5: Procedure
 - 5.1.6: Data Tables
- 5.2: Capacitors and Inductors
 - 5.2.1: Theory Overview
 - 5.2.2: Equipment
 - 5.2.3: Schematics
 - 5.2.4: Procedure
 - 5.2.5: Data Tables
 - 5.2.6: Questions
- 5.3: Introduction to RL and RC Circuits
 - 5.3.1: Theory Overview
 - 5.3.2: Equipment
 - 5.3.3: Components
 - 5.3.4: Schematics
 - 5.3.5: Procedure
 - 5.3.6: Data Tables
 - 5.3.7: Questions
- 5.4: Capacitive Reactance
 - 5.4.1: Theory Overview
 - 5.4.2: Equipment
 - 5.4.3: Components
 - 5.4.4: Schematics
 - 5.4.5: Procedure
 - 5.4.6: Data Tables
 - 5.4.7: Questions
- 5.5: Inductive Reactance
 - 5.5.1: Theory Overview
 - 5.5.2: Equipment
 - 5.5.3: Components
 - 5.5.4: Schematics
 - 5.5.5: Procedure
 - 5.5.6: Data Tables
 - 5.5.7: Questions

6: RLC Circuits and Filtering

- 6.1: Series RLC Circuits
 - 6.1.1: Theory Overview
 - 6.1.2: Equipment
 - 6.1.3: Components
 - 6.1.4: Schematics
 - 6.1.5: Procedure
 - 6.1.6: Data Tables
 - 6.1.7: Questions
- 6.2: Parallel RLC Circuits
 - 6.2.1: Theory Overview
 - 6.2.2: Equipment
 - 6.2.3: Components
 - 6.2.4: Schematics
 - 6.2.5: Procedure
 - 6.2.6: Data Tables
 - 6.2.7: Questions
- 6.3: Series-Parallel RLC Circuits
 - 6.3.1: Theory Overview
 - 6.3.2: Equipment
 - 6.3.3: Components
 - 6.3.4: Schematics
 - 6.3.5: Procedure
 - 6.3.6: Data Tables
 - 6.3.7: Questions
- 6.4: Passive Crossover
 - 6.4.1: Theory Overview
 - 6.4.2: Equipment
 - 6.4.3: Components
 - 6.4.4: Schematics
 - 6.4.5: Procedure
 - 6.4.6: Data Tables
 - 6.4.7: Questions
- 6.5: Series Resonance
 - 6.5.1: Theory Overview
 - 6.5.2: Equipment
 - 6.5.3: Components
 - 6.5.4: Schematics
 - 6.5.5: Procedure
 - 6.5.6: Data Tables
 - 6.5.7: Questions
- 6.6: Parallel Resonance
 - 6.6.1: Theory Overview
 - 6.6.2: Equipment
 - 6.6.3: Components
 - 6.6.4: Schematics
 - 6.6.5: Procedure
 - 6.6.6: Data Tables
 - 6.6.7: Questions

7: Diodes

- 7.1: Diode Curves
 - 7.1.1: Theory Overview
 - 7.1.2: Equipment
 - 7.1.3: Schematics
 - 7.1.4: Procedure
 - 7.1.5: Data Tables
 - 7.1.6: Questions
- 7.2: Light Emitting Diodes
 - 7.2.1: Theory Overview
 - 7.2.2: Equipment
 - 7.2.3: Schematics
 - 7.2.4: Procedure
 - 7.2.5: Data Tables
 - 7.2.6: Questions
- 7.3: Photodiodes
 - 7.3.1: Theory Overview
 - 7.3.2: Equipment
 - 7.3.3: Schematics
 - 7.3.4: Procedure
 - 7.3.5: Data Tables
 - 7.3.6: Questions
- 7.4: The Zener Diode
 - 7.4.1: Theory Overview
 - 7.4.2: Equipment
 - 7.4.3: Schematics
 - 7.4.4: Procedure
 - 7.4.5: Data Tables
 - 7.4.6: Questions
- 7.5: Half-wave Rectifier
 - 7.5.1: Theory Overview
 - 7.5.2: Equipment
 - 7.5.3: Schematics
 - 7.5.4: Procedure
 - 7.5.5: Data Tables
 - 7.5.6: Questions

8: Transistors

- 8.1: Bipolar Junction Transistor- Base Bias - CE Configuration
 - 8.1.1: Theory Overview
 - 8.1.2: Equipment
 - 8.1.3: Schematics
 - 8.1.4: Procedure
 - 8.1.5: Data Tables
 - 8.1.6: Questions
- 8.2: Emitter Bias
 - 8.2.1: Theory Overview
 - 8.2.2: Equipment
 - 8.2.3: Schematics

- 8.2.4: Procedure
- 8.2.5: Data Tables
- 8.2.6: Questions
- 8.3: Voltage Divider Bias
 - 8.3.1: Theory Overview
 - 8.3.2: Equipment
 - 8.3.3: Schematics
 - 8.3.4: Procedure
 - 8.3.5: Data Tables
 - 8.3.6: Questions
- 8.4: Feedback Biasing
 - 8.4.1: Theory Overview
 - 8.4.2: Equipment
 - 8.4.3: Schematics
 - 8.4.4: Procedure
 - 8.4.5: Data Tables
 - 8.4.6: Questions
- 8.5: PNP Transistors
 - 8.5.1: Theory Overview
 - 8.5.2: Equipment
 - 8.5.3: Schematics
 - 8.5.4: Procedure
 - 8.5.5: Data Tables
 - 8.5.6: Questions
- 8.6: Common Emitter Amplifier
 - 8.6.1: Theory Overview
 - 8.6.2: Equipment
 - 8.6.3: Schematics
 - 8.6.4: Procedure
 - 8.6.5: Data Tables
 - 8.6.6: Questions

9: Operational Amplifiers (Op-Amps)

- 9.1: Decibels and Bode Plots
 - 9.1.1: Theory Overview
 - 9.1.2: Reference
 - 9.1.3: Equipment
 - 9.1.4: Components
 - 9.1.5: Schematics
 - 9.1.6: Procedure
 - 9.1.7: Data Tables
 - 9.1.8: Questions
- 9.2: The Differential Amplifier
 - 9.2.1: Theory Overview
 - 9.2.2: Reference
 - 9.2.3: Equipment
 - 9.2.4: Components
 - 9.2.5: Schematics
 - 9.2.6: Procedure
 - 9.2.7: Data Tables

- [9.2.8: Questions](#)
- [9.3: The Non-inverting Voltage Amplifier](#)
 - [9.3.1: Theory Overview](#)
 - [9.3.2: Reference](#)
 - [9.3.3: Equipment](#)
 - [9.3.4: Components](#)
 - [9.3.5: Schematics](#)
 - [9.3.6: Procedure](#)
 - [9.3.7: Data Tables](#)
 - [9.3.8: Questions](#)
- [9.4: The Inverting Voltage Amplifier](#)
 - [9.4.1: Theory Overview](#)
 - [9.4.2: Reference](#)
 - [9.4.3: Equipment](#)
 - [9.4.4: Components](#)
 - [9.4.5: Schematics](#)
 - [9.4.6: Procedure](#)
 - [9.4.7: Data Tables](#)
 - [9.4.8: Questions](#)
- [9.5: The Op Amp Differential Amplifier](#)
 - [9.5.1: Theory Overview](#)
 - [9.5.2: Reference](#)
 - [9.5.3: Equipment](#)
 - [9.5.4: Components](#)
 - [9.5.5: Schematics](#)
 - [9.5.6: Procedure](#)
 - [9.5.7: Data Tables](#)
 - [9.5.8: Questions](#)

[Index](#)

[Glossary](#)

[Detailed Licensing](#)

[Detailed Licensing](#)

Licensing

A detailed breakdown of this resource's licensing can be found in [Back Matter/Detailed Licensing](#).